


Linear wave shaping

.

Linear network Versus Non-linear network



- * Linear n/w is made up of $\rightarrow R, L, C + \text{Active Source.}$
 $\swarrow$
 RC, RL, RLC Linear Components.
- * Non-Linear n/w is made up of $\rightarrow$ Non-linear Components +
 $\swarrow$
 $R, L, C + \text{Active Source.}$
Example - Diode, transistor.

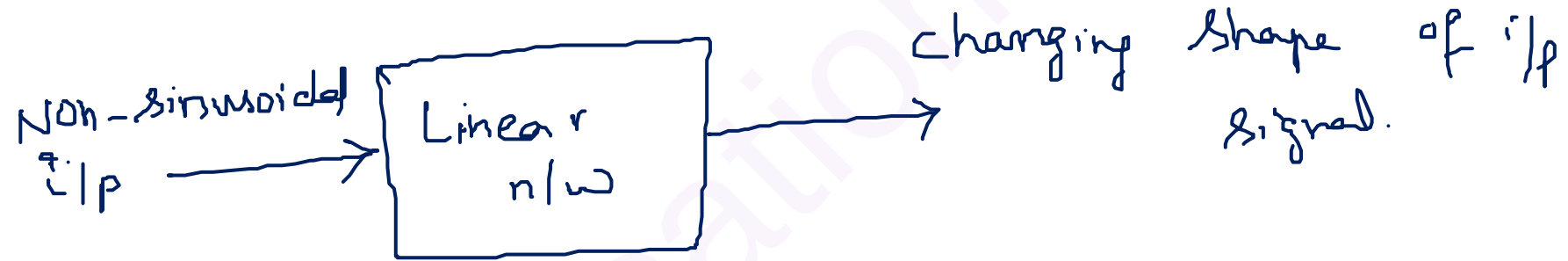Linear Wave Shaping!- The process of changing the shape of a non-sinusoidal signal when passing through a linear n/w.



Linear p/w:-

Low-pass RC network

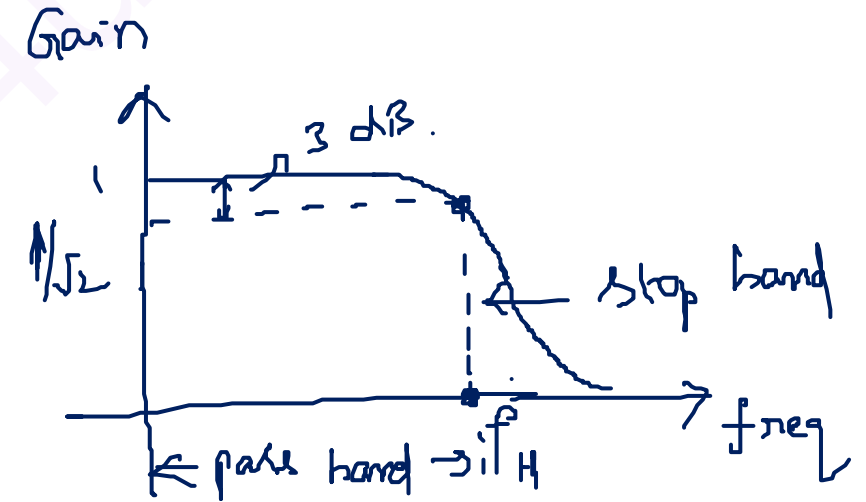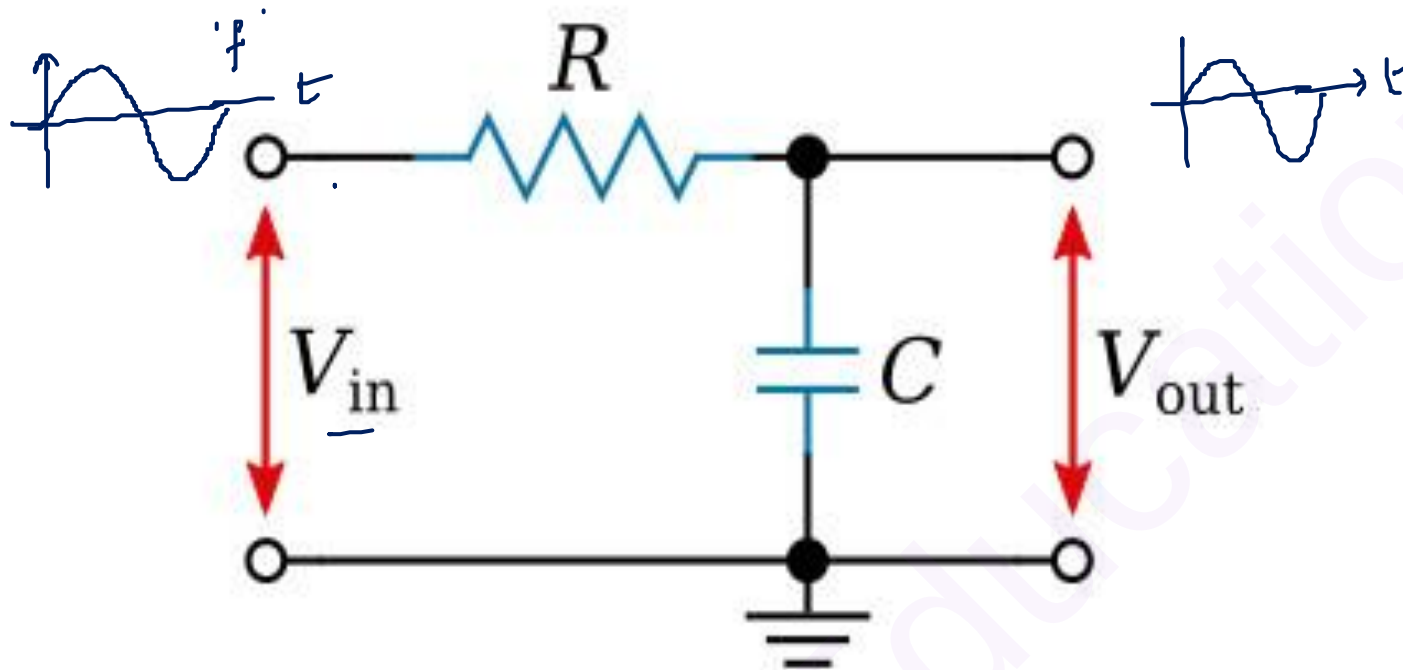

$$|A| = ?$$

$$f_H = ?$$

Gain, $A = \frac{V_o(s)}{V_i(s)}$

$$= \frac{\frac{1}{Cs} \cdot I(s)}{\left(R + \frac{1}{Cs}\right) I(s)}$$


$$= \frac{1}{1 + RCs}$$

We know, $s = j\omega = j 2\pi f$

$$A = \frac{1}{1 + j 2\pi f RC}$$

$$\Rightarrow |A| =$$
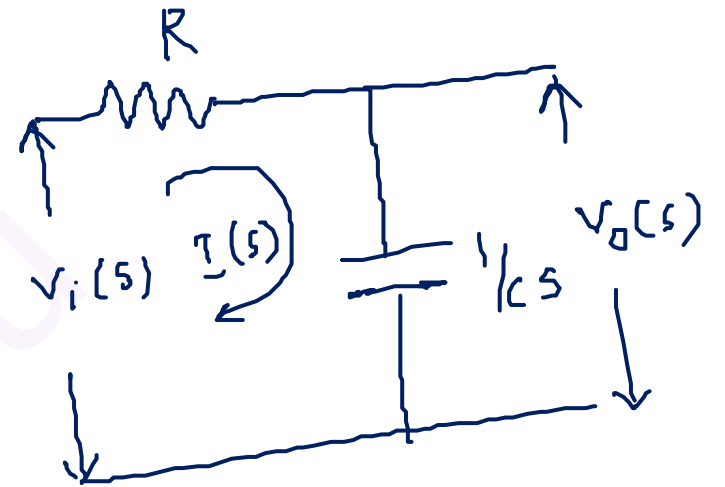
$$\frac{1}{\sqrt{1 + (2\pi f RC)^2}} \quad \text{--- (2)}$$



At frequency, $f = f_H$, $|A| = \frac{1}{\sqrt{2}}$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (2\pi f_H RC)^2}}$$

$$2\pi f_H RC = 1$$

$$f_H = \frac{1}{2\pi RC}$$

from eq. (1) :

$$A = \frac{1}{1 + j \frac{f}{f_H}},$$

$$|A| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

angle, $\theta = \tan^{-1} \left(\frac{f}{f_H} \right)$
=